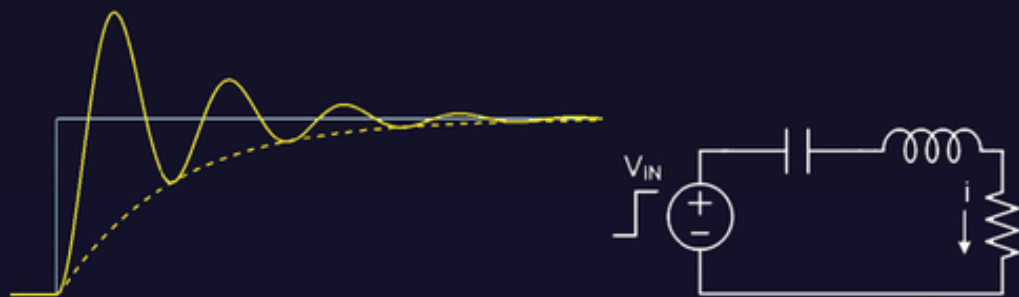


Robert O'Rourke

First and Second Order Circuits and Equations



Technical Background and Insights

First and Second Order Circuits and Equations

IEEE Press
445 Hoes Lane
Piscataway, NJ 08854

IEEE Press Editorial Board
Sarah Spurgeon, *Editor in Chief*

Moeness Amin
Jón Atli Benediktsson
Adam Drobot
James Duncan

Ekram Hossain
Brian Johnson
Hai Li
James Lyke
Joydeep Mitra

Desineni Subbaram Naidu
Tony Q. S. Quek
Behzad Razavi
Thomas Robertazzi
Diomidis Spinellis

First and Second Order Circuits and Equations

Technical Background and Insights

Robert O'Rourke

USA

 **IEEEPress**

WILEY

Copyright © 2024 by The Institute of Electrical and Electronics Engineers, Inc.
All rights reserved.

Published by John Wiley & Sons, Inc., Hoboken, New Jersey.
Published simultaneously in Canada.

No part of this publication may be reproduced, stored in a retrieval system, or transmitted in any form or by any means, electronic, mechanical, photocopying, recording, scanning, or otherwise, except as permitted under Section 107 or 108 of the 1976 United States Copyright Act, without either the prior written permission of the Publisher, or authorization through payment of the appropriate per-copy fee to the Copyright Clearance Center, Inc., 222 Rosewood Drive, Danvers, MA 01923, (978) 750-8400, fax (978) 750-4470, or on the web at www.copyright.com. Requests to the Publisher for permission should be addressed to the Permissions Department, John Wiley & Sons, Inc., 111 River Street, Hoboken, NJ 07030, (201) 748-6011, fax (201) 748-6008, or online at <http://www.wiley.com/go/permission>.

Trademarks: Wiley and the Wiley logo are trademarks or registered trademarks of John Wiley & Sons, Inc. and/or its affiliates in the United States and other countries and may not be used without written permission. All other trademarks are the property of their respective owners. John Wiley & Sons, Inc. is not associated with any product or vendor mentioned in this book

Limit of Liability/Disclaimer of Warranty: While the publisher and author have used their best efforts in preparing this book, they make no representations or warranties with respect to the accuracy or completeness of the contents of this book and specifically disclaim any implied warranties of merchantability or fitness for a particular purpose. No warranty may be created or extended by sales representatives or written sales materials. The advice and strategies contained herein may not be suitable for your situation. You should consult with a professional where appropriate. Neither the publisher nor author shall be liable for any loss of profit or any other commercial damages, including but not limited to special, incidental, consequential, or other damages.

For general information on our other products and services or for technical support, please contact our Customer Care Department within the United States at (800) 762-2974, outside the United States at (317) 572-3993 or fax (317) 572-4002.

Wiley also publishes its books in a variety of electronic formats. Some content that appears in print may not be available in electronic formats. For more information about Wiley products, visit our web site at www.wiley.com.

Library of Congress Cataloging-in-Publication Data

Names: O'Rourke, Robert (Electronic engineer), author.
Title: First and second order circuits and equations : technical background and insights / Robert O'Rourke.
Description: Hoboken, New Jersey : Wiley, [2024] | Includes index.
Identifiers: LCCN 2024008985 (print) | LCCN 2024008986 (ebook) | ISBN 9781119913535 (hardback) | ISBN 9781119913542 (adobe pdf) | ISBN 9781119913559 (epub)
Subjects: LCSH: Electric circuits. | Electronic circuits. | Differential equations.
Classification: LCC TK454 .O75 2024 (print) | LCC TK454 (ebook) | DDC 621.381501/5153--dc23/eng/20240314
LC record available at <https://lccn.loc.gov/2024008985>
LC ebook record available at <https://lccn.loc.gov/2024008986>

Cover Design: Wiley
Cover Image: Courtesy of Robert O'Rourke

Set in 9.5/12.5pt STIXTwoText by Straive, Chennai, India

To my wife Evelyn, whose loving support made this book possible.

Contents

About the Author *xvii*

Acknowledgments *xix*

Part 1 Circuit Elements and Resistive Circuits 1

1	Ohm's Law, Branch Relationships, and Sources	3
1.1	Chapter Summary and Polarity Reference	3
1.1.1	Chapter Summary	3
1.1.1.1	Ohm's Law	3
1.1.1.2	Branch Relationships	4
1.1.2	Polarity Reference	4
1.1.2.1	DC Voltage Source Polarity Example	4
1.1.2.2	DC Current Source Polarity Example	4
1.1.2.3	Reference Polarity versus Physical Current Flow Direction	5
1.2	Branch Relationships and I - V Characteristics	5
1.2.1	Circuit Element Branch Relationships	5
1.2.1.1	Ohm's Law is a Resistor's Branch Relationship	5
1.2.1.2	Capacitor and Inductor Branch Relationships	6
1.2.2	I - V Characteristic Plots	6
1.2.2.1	I - V Characteristics for Circuit Elements	7
1.2.2.2	Resistor I - V Characteristic	7
1.2.2.3	Non-resistor I - V Example	7
1.2.3	Circuit Elements Models and Schematic Symbols	7
1.2.3.1	Circuit Elements are Model Descriptions and Schematic Symbols	7
1.2.3.2	Circuit Schematic Symbols	8
1.3	Ohm's Law, Resistance, and Resistors	8
1.3.1	Resistor and Conductor Equations	8
1.3.1.1	Resistors	8
1.3.1.2	Ohm's Law	8
1.3.1.3	Ohm's Law Notation with Time-Dependent Functions	8
1.3.2	Impedance and Ohm's Law Beyond Resistive Circuits	9
1.3.3	Resistance and Bulk Resistivity	9
1.3.3.1	Bulk Resistivity and Resistance	10

1.4	Current, Voltage, and Sources Overview	11
1.4.1	Description and Units of Current and Voltage	11
1.4.2	Current and Voltage Source Definitions	11
1.4.3	Current and Voltage Source Branch Relationships	11
1.5	Voltage Sources	12
1.5.1	Independent Voltage Source Schematic symbols	12
1.5.2	Independent Voltage Source Branch Relationship (I - V Characteristic)	12
1.5.3	Intuitive Description of an Independent Voltage Source	13
1.6	Current and Current Sources	14
1.6.1	Electrical Current	14
1.6.1.1	Description and Definition of Electrical Current	14
1.6.1.2	Units of Current and Charge	14
1.6.1.3	Positive Current Convention	14
1.6.2	Current Sources	14
1.6.2.1	Independent Current Source Definition	14
1.6.2.2	Alternative Independent Current Source Schematic Symbol	15
1.6.2.3	Current Source Water Analogy	15
1.6.2.4	Current Sources Can't Be Open Circuit	15
1.6.3	Current Source Branch Relationship (I - V Characteristic)	15
2	Kirchhoff's Laws and Resistive Dividers	17
2.1	Kirchhoff's Laws and Dividers Comparison Summary	17
2.2	Kirchhoff's Laws Physical Analogies	18
2.2.1	Kirchhoff's Voltage Law – Gravitational (Elevation) Analogy	18
2.2.1.1	Voltage Doesn't Accumulate Around a Loop	19
2.2.2	Kirchhoff's Current Law – Water Analogy	19
2.2.2.1	Current Doesn't Accumulate in a Node	19
2.2.2.2	Water and Current Flow in a Loop	19
2.3	Source Polarity in KVL – Time and Frequency Domains	19
2.3.1	DC Source Polarity and Kirchhoff's Voltage Law	19
2.3.1.1	Positive Current Convention Distinction	20
2.3.2	Time Domain Current Source Reference Polarity Example	20
2.3.2.1	Circuit Simulation Results	20
2.3.3	Time Domain Voltage Source Reference Polarity Example	21
2.3.3.1	Circuit Simulation Results – Time Domain Voltage Source	21
2.3.4	Frequency Domain Current Source Reference Polarity Example	22
2.3.4.1	Circuit Simulation Results – Frequency Domain Current Source	22
2.3.5	Frequency Domain Voltage Source Reference Polarity Example	23
2.3.5.1	Circuit Simulation Results – Frequency Domain Voltage Source	24
2.4	Formulae Summary for Resistors in Series and Parallel	26
2.5	Resistors in Series	27
2.5.1	Derivation of the Formulae for Two Resistors in Series	28
2.5.2	n Resistors in Series	28
2.5.3	Conductors in Series	29
2.5.3.1	Admittance is the Inverse of Impedance	29
2.5.3.2	First Derivation of the Formula for the Conductance of Two Resistors in Series	29
2.5.3.3	Second Derivation of the Formula for the Conductance of Two Resistors in Series	30
2.5.4	Impedances in Series	31
2.5.4.1	Impedance Z in Either s or $j\omega$ Frequency Domains	31
2.5.4.2	Susceptance B	31
2.6	Voltage Dividers	32

2.6.1	Calculation of the Voltage Divider Output Voltage v_{out}	32
2.6.2	Voltage Divider for Generalized Impedance	32
2.7	Parallel Circuit Element Formulae	33
2.7.1	Derivation of the Formulae for Two Resistors in Parallel	33
2.7.2	Derivation of the Formula for n Resistors in Parallel	34
2.7.3	Conductance in Parallel	35
2.7.3.1	Admittance in Parallel	35
2.7.4	Impedance in Parallel	35
2.8	Current Dividers	36
2.8.1	Derivation of Current Divider Formula for Two Resistors	36
2.8.1.1	Current Divider Formulae	36
2.8.2	Alternate Derivation of Current Divider Formula	36
2.8.2.1	Current Divider Formula	37
2.8.3	The Current Divider Formula Generalizes to Impedances	37
2.8.3.1	Current Divider Formulae	37
2.9	Current and Voltage Intuitions	37
2.9.1	Only One Current in a Series Circuit	38
2.9.2	Only One Voltage in a Parallel Circuit	38
3	Opamp Models and Resistive Circuits	39
3.1	Introduction and Ideal Opamp Model Results Overview	39
3.1.1	Ideal Opamp Inverting Amplifier Circuit Results Summary	39
3.1.1.1	Ideal Opamp Non-Inverting Amplifier Results Summary	40
3.1.2	Opamp Models	40
3.1.2.1	Standard Opamp Model	40
3.1.2.2	Voltage-Controlled Voltage Source Opamp Model	40
3.1.2.3	Ideal Opamp Model	41
3.2	Ideal Opamp Resistive Amplifier Circuits	41
3.2.1	Inverting Amplifier Circuit Ideal Opamp Analysis	41
3.2.2	Non-Inverting Amplifier Circuit Ideal Opamp Analysis	42
4	Reactive Circuit Elements	45
4.1	Capacitor and Inductor Comparison Summary	45
4.2	Capacitors	47
4.2.1	The Capacitor Circuit Element	47
4.2.1.1	Capacitor Branch Relationships	47
4.2.2	Capacitors in Series and Parallel	48
4.2.2.1	Parallel Capacitances	48
4.2.2.2	Intuitive Memory Aid for Parallel Capacitance	48
4.2.2.3	Capacitor Series Connections	49
4.2.2.4	Intuitive Memory Aid for Series Capacitance	49
4.2.3	Capacitor Time Domain Behavior	49
4.2.3.1	Hydraulic Analogy for Capacitance	49
4.2.4	Capacitor Voltage Phase Lags Current Phase	50
4.3	Inductors	51
4.3.1	The Inductor Circuit Element	51
4.3.1.1	Inductor Branch Relationships	51
4.3.2	Inductors in Series and Parallel	52
4.3.2.1	Inductor Series Connections	52
4.3.2.2	Intuitive Memory Aid	52
4.3.2.3	Inductor Parallel Connections	53

- 4.3.3 Inductor Time Domain Behavior 53
- 4.3.3.1 Hydraulic Analogy for Inductance 53
- 4.3.4 Time and Frequency – Inductor Voltage Phase Leads Current Phase 54

Part 2 First-Order Circuits 57

- 5 First-Order RC and RL Circuits Introduction 59**
 - 5.1 What are First-Order Circuits? 59
 - 5.1.1 A Capacitor or an Inductor Makes a First-Order Circuit 59
 - 5.1.2 First-Order Circuits Can Filter in the Frequency Domain 59
 - 5.1.3 First-Order Circuits Are Described by First-Order Differential Equations 60
 - 5.1.4 First-Order Circuit Exponential Step Responses in Time Domain 60
 - 5.2 Intuitive First-Order Circuit Frequency Domain Examples 61
 - 5.3 First-Order Natural and Step Response Overview 62
 - 5.3.1 First-Order RC and RL Natural Response 62
 - 5.3.2 Intuitive Analysis of First-Order RC and RL Step Response 63
- 6 First-Order Frequency Domain Response 65**
 - 6.1 First-Order Frequency Response Overview 65
 - 6.1.1 Frequency Response Notations and Complex Magnitude 65
 - 6.1.1.1 Complex Magnitude 65
 - 6.1.1.2 Frequency Domain Transfer Function Magnitude Bode Plots 66
 - 6.1.1.3 Frequency Domain Transfer Function Phase Calculation 67
 - 6.1.1.4 Frequency Domain Response Topology Examples 67
 - 6.1.1.5 First-Order Frequency Response Formulae with ω_0 69
 - 6.1.1.6 First-Order Corner Frequency and Half-Power Calculations 70
 - 6.2 Series RC High-pass Filter Frequency Response 71
 - 6.2.1 Series RC Frequency Domain Results Overview 71
 - 6.2.2 Series RC Frequency Domain Example Intuitive Analysis 72
 - 6.2.2.1 Lead Network 74
 - 6.2.3 Series RC Frequency Domain Transfer Function Calculation 74
 - 6.2.3.1 Calculating the Transfer Function 74
 - 6.2.4 Series RC Transfer Function Magnitude Calculation 75
 - 6.2.4.1 Transfer Function Magnitude at the Corner Frequency 76
 - 6.2.4.2 Alternate Form of Magnitude of the Transfer Function 77
 - 6.2.5 Series RC Magnitude Bode Diagram Calculation 77
 - 6.2.6 Series RC Magnitude Bode Diagram Plot 79
 - 6.2.6.1 Calculate the High-Frequency 0 dB Asymptote 79
 - 6.2.6.2 Plot the High-Frequency 0 dB Asymptote 79
 - 6.2.6.3 Calculate the Low-Frequency Asymptote 79
 - 6.2.6.4 Plot the Low-Frequency Asymptote 80
 - 6.2.6.5 20 dB per Decade Roll Up Illustration 81
 - 6.2.6.6 Corner Frequency 81
 - 6.2.6.7 Transfer Function dB Magnitude at the Corner Frequency 81
 - 6.2.7 Series RC Transfer Function Phase Calculation 83
 - 6.2.7.1 Calculating the Phase Response of a Complex Transfer Function 84
 - 6.2.8 Series RC Phase Bode Diagram Calculation 85
 - 6.2.8.1 Phase as ω Approaches 0 85

6.2.8.2	Phase as ω Approaches Infinity	85
6.2.8.3	Phase at Corner (Break) Frequency $\omega = \omega_0 = 1/RC$	85
6.2.9	Series RC Phase Bode Diagram Plot	86
6.2.10	Series RC High-pass Filter Phase Relationships	87
6.2.10.1	Phasor Diagram at Corner Frequency	87
6.3	Series RL Low-pass Filter Frequency Response	89
6.3.1	Series RL Frequency Domain Results Overview	89
6.3.2	Series RL Frequency Domain Example Intuitive Analysis	91
6.3.2.1	Lag Network	92
6.3.3	Series RL Frequency Domain Transfer Function Calculation	92
6.3.3.1	Calculating the Transfer Function $\frac{V_{out}}{V_s}$	92
6.3.3.2	Calculating the Magnitude of the Transfer Function – Summarized	93
6.3.3.3	Phase of the RL Low-pass Filter Transfer Function	94
6.3.3.4	Calculating the Phase of the Transfer Function – Summarized	94
6.3.4	Series RL Low-pass Filter Phase Relationships	95
6.3.4.1	Phasor Diagram at Corner Frequency	95
6.3.5	Series RL Transfer Function Magnitude – Detailed Calculation	97
6.3.6	Series RL Magnitude Bode Diagram Calculation	97
6.3.7	Series RL Magnitude Bode Diagram Plot	99
6.3.7.1	Calculate the High-Frequency Asymptote	99
6.3.7.2	Plot the High-Frequency Asymptote	100
6.3.7.3	Graph of the High-Frequency Asymptote	100
6.3.7.4	Illustrating the -20 dB per Decade Roll Off	100
6.3.7.5	Low-Frequency Asymptote for the Magnitude Bode Diagram	101
6.3.7.6	Corner Frequency	102
6.3.8	Series RL Transfer Function Phase – Detailed Calculation	104
6.3.8.1	Constructing the Transfer Function Phase Bode Diagram	106
6.3.8.2	Phase as ω Approaches 0	106
6.3.8.3	Phase as ω Approaches Infinity	106
6.3.8.4	Phase at Corner (Break) Frequency $\omega = \omega_0 = R/L$	106
6.4	Series RC Low-pass Filter Frequency Response	108
6.4.1	Series RC Frequency Domain Results Overview	108
6.4.2	Series RC Frequency Domain Example Intuitive Analysis	110
6.4.2.1	Lag Network	111
6.4.3	Series RC Frequency Domain Transfer Function Calculation	111
6.4.3.1	Calculating the Transfer Function	111
6.4.4	Series RC Transfer Function Magnitude Calculation	112
6.4.4.1	Calculating the Transfer Function Magnitude in dB	113
6.4.5	Series RC Transfer Function Phase Response Calculation	114
6.4.6	Series RC Low-pass Filter Phase Relationships	116
6.4.6.1	Phasor Diagram at Corner Frequency	116
6.5	Series RL High-pass Filter Frequency Response	118
6.5.1	Series RL Frequency Domain Results Overview	118
6.5.2	Series RL Frequency Domain Example Intuitive Analysis	120
6.5.2.1	Lead Network	121
6.5.3	Series RL Frequency Domain Transfer Function Calculation	121
6.5.3.1	Calculating the Transfer Function $\frac{V_{out}}{V_s}$	121
6.5.4	Series RL Transfer Function Magnitude Calculation	122
6.5.4.1	Series RL Bode Plot Calculations	123

6.5.5	Series RL Transfer Function Phase Response Calculation	124
6.5.5.1	Calculating the Phase Response of a Complex Transfer Function	125
6.5.6	Series RL Low-pass Filter Phase Relationships	126
6.5.6.1	Phase Relationships and Phasors at the Corner Frequency	127
6.6	Parallel RL Low-pass Filter Frequency Response	128
6.6.1	Parallel RL Frequency Domain Results Overview	128
6.6.2	Parallel RL Frequency Domain Example Intuitive Analysis	130
6.6.2.1	Lag Network I_{out}/I_S	131
6.6.2.2	Transfer Impedance V_{out}/I_S	131
6.6.3	Parallel RL Current Transfer Function Calculation	132
6.6.3.1	Calculating the Current Low-pass Filter Transfer Function	132
6.6.3.2	Alternate Calculation of the Current Transfer Function I_{out}/I_S	133
6.6.4	Parallel RL Current Transfer Function Magnitude Calculation	134
6.6.5	Parallel RL Current Transfer Function Phase Calculation	135
6.6.5.1	Calculating the Phase Response of a Complex Transfer Function	135
6.6.6	Parallel RL Impedance Transfer Function Calculation	136
6.6.6.1	Calculate the RL Circuit Impedance Transfer Function $\frac{V_{out}}{V_S}$	136
6.6.7	Parallel RL Current Phasor Diagrams – Lag Network	137
6.7	Parallel RC High-pass Filter Frequency Response	139
6.7.1	Parallel RC Frequency Domain Results Overview	139
6.7.2	Parallel RC Frequency Domain Example Intuitive Analysis	141
6.7.3	Parallel RC Current Transfer Function Calculation	142
6.7.3.1	Calculating the Current High-pass Filter Transfer Function	142
6.7.4	Parallel RC Input Impedance Calculation	143
6.7.5	Parallel RC Current Transfer Function Magnitude Calculation	144
6.7.6	Parallel RC Current Transfer Function Phase Calculation	144
6.7.7	Parallel RC Phasor Diagrams – Lead Network	146
7	Discharging and Charging First-Order RC and RL Circuits	149
7.1	Discharging RC and RL Circuits – Natural Response	149
7.1.1	Discharging Circuits with Switches	149
7.1.2	Circuit Topologies Before Switching	151
7.1.3	Circuit Topologies After Switching – Natural Response	151
7.2	Charging RC and RL Circuits – Step Response	153
7.2.1	Charging Circuits with Switched Sources	153
7.2.2	Step Response Curves and Equations	154
7.3	The Exponential Time Constant τ (Tau)	155
7.4	Pulse Train Time Constants Simulation Example	156
8	Natural Response of RC and RL Circuits	159
8.1	RC and RL Circuits Natural Response Summary	159
8.2	RC and RL Natural Response Derivation	160
8.2.1	Two Single-Pole Single-Throw Switches for Natural Response	160
8.2.2	RC and RL ZIR Differential Equation Derivation	161
8.2.3	RC and RL ZIR Differential Equation Solutions	162
8.2.4	Alternative Derivation of RC and RL ZIR Differential Equations	164
8.3	RC Natural Response (ZIR) Time Constants and Initial Current	166
8.3.1	Slope of Exponential Function at time 0	166
8.3.2	Solve for the X-Intercept	167
8.4	Natural Response of Series RL with Voltage Source	167

8.4.1	Generating Series RL Initial Conditions with Switches	168
8.4.2	Series RL Natural Response Differential Equation Solution	168
8.5	First-Order RC and RL Natural Response Summary	171
9	First-Order Step Response of RC and RL Circuits	173
9.1	First-Order Step Response Summary Overview	173
9.1.1	Step Response Introduction	173
9.1.2	Differential Equation Solution Using a Particular Solution	173
9.1.3	Step Response Topology Summary	174
9.1.4	First-Order Step Response Equation Summary	175
9.1.5	Overview of Step Response of Series RL with Voltage Source	176
9.2	Intuitive Analysis of RC and RL Step Response	177
9.2.1	Step Response Intuitive Analysis Setup	177
9.2.2	Step Response Branch Relationship Intuition	178
9.2.3	Step Response Intuitive Analysis Results	179
9.2.3.1	Equivalent Circuits – Same Voltage Response	180
9.3	Series RC Step Response Solution Using a Particular Solution	181
9.3.1	Natural Response of the Homogeneous RC Circuit	182
9.3.2	Generate a Particular Solution from a Constant Function	183
9.4	Series RL Step Response Solution Using a Particular Solution	184
9.4.1	Natural Response of the Homogeneous RL Circuit	185
9.4.2	Generate a Particular Solution from a Constant Function	186
9.5	Series RL Step Response with Voltage Source	188
9.6	First-Order Step Response Summary	190
10	Complete Response of First-Order RC and RL Circuits	191
10.1	First-Order Complete Response Summary Overview	191
10.1.1	Complete Response Definition Equations	191
10.1.2	Complete Response RC and RL Results	191
10.2	Series RC Complete Response Examples	192
10.2.1	First RC Example – No Initial Capacitor Voltage	193
10.2.2	Second RC Example – Plus 0.5 V Initial Capacitor Voltage	194
10.2.3	Third RC Example – Minus 0.5 V Initial Capacitor Voltage	195
10.3	RL Complete Response Example and Intuitive Analysis	195
10.3.1	First RL Example – No Initial Inductor Current	196
10.3.2	Second RL Example – Additive Initial Current	197
10.3.3	Third RL Example – Subtractive Initial Current	198
10.4	Complete Response with Switches	199
10.4.1	Switch Models for Complete Response	199
10.4.2	RC Complete Response Derivation with Direct Integration	199
10.4.3	RL Complete Response Derivation with Direct Integration	201
10.5	Complete Response General Derivation and Formulae	202
11	First-Order Opamp Integrator and Differentiator Circuits	207
11.1	RC Integrator Circuit Step Response	207
11.1.1	Description of Step Response	208
11.2	Opamp Integrator Circuit	208
11.2.1	Ideal Opamp Model Summary	208
11.2.2	Ideal Opamp Integrator Circuit Intuitive Analysis	209
11.2.3	Ideal Opamp Integrator Circuit Derivation	209
11.3	Opamp Inverting Differentiator Circuit	210
11.3.1	Ideal Opamp Differentiator Circuit Derivation	210

	Part 3	Second-Order Circuits	211
12	Second-Order RLC Circuits Overview		213
12.1	What are Second-Order Circuits?		213
12.1.1	A Capacitor and an Inductor Together Make a Second Order Circuit		213
12.1.2	RLC Circuits Have a Resonant Frequency		213
12.1.3	Second-Order Circuit Differential Equations		214
12.1.4	Second-Order Circuits Can Exhibit Overshoot and Ringing		215
12.2	Resonance in the Frequency Domain		215
12.2.1	Series and Parallel Impedances		215
12.2.2	Circuit Elements Around Resonance		216
12.3	Second-Order RLC Transfer Functions and Q		216
12.3.1	Second-Order Transfer Functions		216
12.3.2	Quality Factor Q		217
12.4	Two Time Domain Responses		217
12.4.1	RLC Natural Response 3 Cases		217
12.4.2	RLC Step Response 3 Cases		218
12.4.3	Complete Response is ZIR Plus ZSR		218
13	Second-Order RLC Frequency Response		219
13.1	Series and Parallel RLC Impedance		219
13.1.1	Series and Parallel Impedance Summary		219
13.1.1.1	Current Flow Above and Below Resonance		220
13.1.2	Series RLC Impedance and Resonant Frequency		221
13.1.2.1	Magnitude of Series RLC Impedance		222
13.1.2.2	Resonance of Series RLC Impedance		222
13.1.2.3	Series RLC Impedance Intuition		223
13.1.3	Series RLC Impedance Magnitude and Resonant Frequency Example		223
13.1.4	Parallel RLC Impedance and Resonant Frequency		225
13.1.4.1	Magnitude of Parallel RLC Impedance		226
13.1.5	Parallel RLC Admittance		227
13.1.5.1	Resonance of Parallel RLC		227
13.1.5.2	Parallel RLC Impedance Intuition		229
13.2	Second-Order RLC Frequency Response		229
13.2.1	Second-Order Series RLC Voltage Transfer Function		229
13.2.1.1	Another Form of the Series RLC Transfer Function		230
13.2.1.2	Magnitude of Series RLC Transfer Function		231
13.2.1.3	Phase of Series RLC Transfer Function		231
13.2.1.4	Phase of Another Form of Series RLC Transfer Function		232
13.2.2	Series RLC Transfer Function Magnitude and Phase Simulation Example		233
13.2.3	Second-Order Parallel RLC Current Transfer Function		234
13.2.3.1	Magnitude of the Parallel RLC Current Transfer Function		235
13.2.3.2	Phase of Parallel RLC Current Transfer Function		236
13.2.4	Parallel RLC Impedance Magnitude and Phase Simulation Example		237
13.3	Second-Order RLC Bandwidth and Quality Factor		238
13.3.1	Series RLC Bandwidth		238
13.3.2	Series RLC Bandwidth Example		239
13.3.2.1	10Ω Widens Bandwidth		240
13.3.3	Parallel RLC Bandwidth		240
13.3.4	Parallel RLC Bandwidth Example		241
13.3.4.1	3Ω Widens Bandwidth		243

13.3.5	Quality Factor Q	243
13.3.6	Series RLC Quality Factor Q	244
13.3.6.1	Series RLC Equations for Q	244
13.3.6.2	Series RLC Q and Bandwidth Intuition	244
13.3.6.3	Series RLC Transfer Function in Terms of Q	245
13.3.6.4	Series RLC Transfer Function Magnitude in Terms of Q	245
13.3.6.5	Series RLC Transfer Function Phase in Terms of Q	246
13.3.6.6	Express Series RLC Bandwidth Cutoff Frequencies in Terms of Q	247
13.3.7	Parallel RLC Quality Factor Q	247
13.3.7.1	Parallel RLC Equations for Q	247
13.3.7.2	Parallel RLC Q and Bandwidth Intuition	248
13.3.7.3	Parallel RLC Transfer Function in Terms of Q	248
13.3.7.4	Parallel RLC Transfer Function Magnitude in Terms of Q	249
13.3.7.5	Parallel RLC Transfer Function Phase in Terms of Q	249
13.3.7.6	Express Parallel RLC Bandwidth Cutoff Frequencies in Terms of Q	250
14	Second-Order RLC Circuit Natural Response	251
14.1	Second-Order Natural Response Introduction	251
14.1.1	Second-Order Natural Response Overview	251
14.1.2	Second-order RLC Analysis Outline	251
14.1.2.1	Set Up the Differential Equations from KCL or KVL	252
14.1.2.2	Solve for the Characteristic Equation	252
14.1.2.3	Generate the Characteristic Roots	252
14.1.2.4	Conditions for Four Cases of Characteristic Roots	253
14.1.2.5	General Solution Form	254
14.2	Second-order Natural Response in Terms of R , L , and C	254
14.2.1	Second-order RLC Differential Equations	254
14.2.2	Second-order RLC Differential Equation Solutions	256
14.2.3	Roots of the Second-order Characteristic Equations	257
14.2.3.1	Changing the Form of the Parallel RLC Roots Equations with R	258
14.2.3.2	Calculating Two Forms of RLC Roots Equations	260
14.2.4	Summary of RLC Differential Equations Solutions so Far	261
14.2.5	Four Cases of Characteristic Roots and RLC Response	262
14.2.6	Series RLC Critical Damping Resistance Calculation Example	267
14.2.6.1	Calculate the Critical Damping Resistance	268
14.2.7	Parallel RLC Critical Damping Resistance Calculation Example	268
14.2.7.1	Calculate Critical Damping for a Parallel RLC Example	269
14.2.8	Calculating Constants for the RLC General Solutions	269
14.2.8.1	Calculation of K_1 and K_2 for Overdamped RLC	270
14.2.8.2	Overdamped Series RLC $i'(0)$ Substitution for K_1 and K_2 Calculation	272
14.2.8.3	Overdamped Parallel RLC $i'(0)$ Substitution for K_1 and K_2 Calculation	273
14.2.8.4	The Function $tKe^{s_2 t}$ for Critically Damped RLC	273
14.2.8.5	Calculation of K_1 and K_2 for Critically Damped RLC	274
14.2.8.6	Calculation of K_1 and K_2 for Critically Damped Series RLC	274
14.2.8.7	Calculation of K_1 and K_2 for Critically Damped Parallel RLC	275
14.2.8.8	Calculation of K_1 and K_2 for Underdamped RLC	276
14.2.8.9	Calculation of K_1 and K_2 for Oscillatory Lossless RLC Natural Response	280
14.2.9	Series RLC ZIR Differential Equations – $v_C(t)$ and $i(t)$	281
14.2.10	Parallel RLC ZIR Differential Equations – $v(t)$ and $i_L(t)$	282
14.3	Second-order Damping Variables α and ω_0	283
14.3.1	Second-order Damping and Frequency Variables Overview	283

14.3.2	Second-order Differential Equations with Variables α and ω_0	284
14.3.3	Alpha and Omega Variables for 2nd-order Characteristic Roots	285
14.3.4	Four Cases of Characteristic Roots in Terms of α	287
14.3.5	Q and ω_d	289
14.3.6	Second-order Root Locus - α and ω_0	290
14.4	Second-order Damping Ratio ζ – Zeta	291
14.4.1	Introduction to RLC Damping Ratio ζ	291
14.4.2	Damping Ratio ζ and Critical Damping	292
14.4.3	RLC Differential Equation Analysis in Terms of ζ	293
14.4.4	Four Cases of Characteristic Roots in Terms of ζ	295
14.4.5	Second-order Root Locus with ζ	296
15	Second-Order RLC Step and Complete Response	299
15.1	RLC Step Response Intuitive Overview	299
15.1.1	Series RLC Branch Relationship Intuition	299
15.1.2	Series RLC Step Response Simulation Example	300
15.2	RLC Step Response Detailed Analyses	301
15.2.1	Step Response Detailed Description	301
15.2.2	RLC Step Response Homogeneous Differential Equation Solution	302
15.2.3	Particular Solution to the Non-Homogeneous Differential Equation	303
15.3	Parallel RLC Intuitive Step Response Example	303
15.4	Complete RLC Time Domain Response	305
15.4.1	RLC Complete Response is ZSR Plus ZIR	305
15.4.2	RLC Complete Response Simulation Example	305
Part 4 Technical Background Topics		307
16	Complex Numbers, Exponentials, and Phasors	309
16.1	Imaginary and Complex Numbers	309
16.1.1	Imaginary Operators and Complex Numbers	309
16.1.2	The Complex Plane and Polar Notation	310
16.1.2.1	Alternative Expressions for the Complex number z	311
16.2	Exponentials, Complex Numbers, and Trigonometry	311
16.2.1	The Unit Circle and Trigonometry	311
16.2.2	The Complex Conjugate	312
16.2.3	Complex Numbers and Functions	313
16.2.3.1	Complex Functions	313
16.2.3.2	Magnitude and Phase Calculations	313
16.3	Phasors and Sinusoidal Steady State	314
16.3.1	Phasors Allow Algebraic Analysis of Reactive Circuits	314
16.3.2	Phasor Derivation from Sine or Cosine	314
16.3.3	Sinusoidal Steady-State Frequency Domain	315
16.3.4	Rotating Phasor $e^{j\omega t}$	316
16.3.5	Sinusoidal Phase and Phasor Diagrams	317
16.3.6	Phasor Properties Summary	317
Index		319

About the Author

Robert O'Rourke has an electrical engineering degree from UC Berkeley, including coursework in circuit theory and electromagnetics. Robert has taught electronics and calculus at college level. Robert worked with circuit theory and circuit and system simulation at Analog, now a part of Synopsys, Inc. During several positions in his career, Robert hired and managed electronic engineers in applications engineering roles that involved circuit theory. Robert has taught circuit and electromagnetic simulation training courses for multiple vendors. As part of Ansys, Robert also created circuit and electromagnetic simulation product training courses for the Ansys Learning Hub.

Acknowledgments

The simulations made for this book and the simulation schematics and graphs appearing in this book were made with the QUCS simulator, available from [SourceForge.net](https://sourceforge.net/projects/qucs/).

The author would also like to thank Professor Alberto Sangiovanni-Vincentelli, who first taught him circuit theory at UC Berkeley.

Part 1

Circuit Elements and Resistive Circuits

1

Ohm's Law, Branch Relationships, and Sources

1.1 Chapter Summary and Polarity Reference

1.1.1 Chapter Summary

Ohm's law describes the relationship between voltage, current, and resistance for resistive circuits. This chapter describes Ohm's law and the related circuit elements, resistors, current sources, and voltage sources. This chapter also covers the more general idea of branch relationships, the relation between the voltage across a circuit element and the current through a circuit element, for resistors, voltage sources, and current sources.

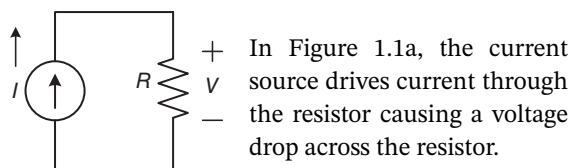
Current source and resistor

Figure 1.1a Current source driving a resistor.

The ideal independent **current source** supplies a fixed amount of current I through the resistor R regardless of the amount of voltage across the source.

The resistor R resists the flow of current through it. The amount of voltage V , that develops across the resistor R , as a result of the current I flowing through the resistor R , is determined by Ohm's law, V equals IR , shown in Equation 1.1a

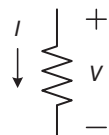
1.1.1.1 Ohm's Law

Figure 1.2 Resistor schematic symbol with passive sign convention.

The voltage across a resistor, shown in Figure 1.2, equals the current through the resistor times the resistance of the resistor.

$$V = IR$$

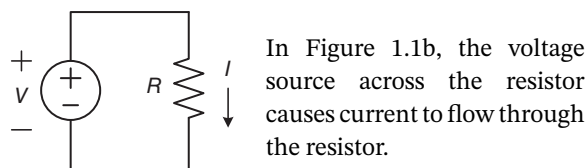
Voltage source and resistor

Figure 1.1b Voltage source across a resistor.

The ideal independent **voltage source** supplies a fixed amount of voltage V across the resistor R regardless of the amount of current through the source.

The resistor R resists the flow of current through it. The amount of current, that flows through the resistor, as a result of the voltage V across the resistor R , is determined by Ohm's law, I equals V over R , shown in Equation 1.1b.

The current through a resistor equals the voltage across the resistor divided by the resistance of the resistor.

$$I = V/R$$

$$(1.1b)$$

1.1.1.2 Branch Relationships

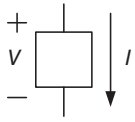


Figure 1.3 Passive sign convention on a generic fictitious schematic symbol.

The branch relationship is the equation describing the relationship between current through a circuit element (in a branch of a circuit) and the voltage across the circuit element. For example, Ohm's law $V = IR$ or $I = V/R$ is the branch relationship of a resistor. Figure 1.3, with a simple square shape, is a generic, non-specific circuit element.

1.1.2 Polarity Reference

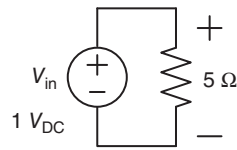


Figure 1.4a 1 volt DC voltage source across a 5 ohm resistor.

In Figure 1.4a, 1 V divided by 5 Ω equals 200 mA (0.2 A).

In each of these two direct current (DC) examples, Figures 1.4a and 1.4b, the current in the loop is 200 mA DC, going down through the resistor from + to -, and the voltage across the 5 Ω resistor is 1 V DC.


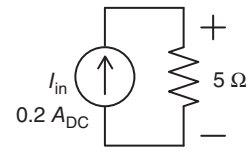


Figure 1.4b 200 mA DC current source driving a 5 ohm resistor.

In Figure 1.4b, 0.2 A multiplied by 5 Ω equals 1 V.

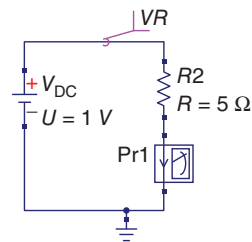1.1.2.1 DC Voltage Source Polarity Example



Number	Pr1.I	VR.V
1	0.2	1

Figure 1.5 Circuit simulation schematic with a voltage source and a resistor.


The voltage source in Figure 1.4a applies voltage across the resistor, and the + (plus) and - (minus) signs on the resistor indicate the polarity of the voltage.

Figure 1.5 shows a circuit simulation schematic corresponding to the circuit in Figure 1.4a. The voltage source symbol in Figure 1.5 is specific to DC voltage sources.

There is a current meter in the right-hand leg of the circuit, just below the resistor. The downward arrow in the current meter symbol indicates a reference direction pointing down; the current meter considers clockwise flow of current in the circuit to be positive.

For the DC circuit simulation, there is a table of results in Figure 1.5. VR, measured at the top of the circuit, is positive 1 V, and the current Pr1.I, measured by the current meter, is 200 mA, verifying that current flows downward through the resistor.

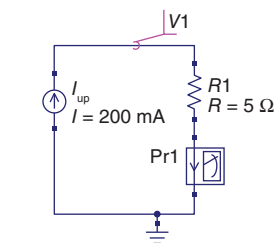1.1.2.2 DC Current Source Polarity Example



Number	Pr1.I	V1.V
1	0.2	1

Figure 1.6 Circuit simulation schematic with a current source and a resistor.

The arrow, pointing up in the current source in Figure 1.4b, indicates the direction of a positive current from the source. Applying Ohm's law, multiplying the current times the resistance, tells us the voltage across the resistor, both the amount and the polarity of the voltage. The + (plus) and - (minus) signs on the resistor indicate the polarity of the voltage.

Figure 1.6 shows a circuit simulation schematic corresponding to the circuit in Figure 1.4b. The downward arrow in the current meter symbol indicates a reference direction pointing down; the current meter considers clockwise flow of current in the circuit to be positive.

In Figure 1.6, the current source arrow points up, telling us that current flows up and out of the current source, and then down through the resistor. As expected from Ohm's law, 200 mA multiplied by $5\ \Omega$ yields 1 mV across the resistor. This 1 V result appears in the table under V1.V. The current direction of the current source and the current meter are the same, and the measured current, under Pr1.I, is positive 200 mA.


At the top of the schematic in Figure 1.6, there is a V1 marker, indicating a voltage measurement. This voltage is referenced to ground, so it is equivalent to the way schematics show a + (plus) sign above the resistor and a - (minus) sign below the resistor.

In Figure 1.7 the current source arrow points down, telling us that current flows down and out of the current source, and then up through the resistor, the opposite direction from the current source in Figure 1.6.

This makes the measured voltage V2.V -1 V, as it is referenced from the top V2 voltage reference.

As expected from Ohm's law, $-0.2\ \text{A}$ multiplied by $5\ \Omega$ yields $-1\ \text{V}$ across the resistor. This result appears under V2.V in units of volts.

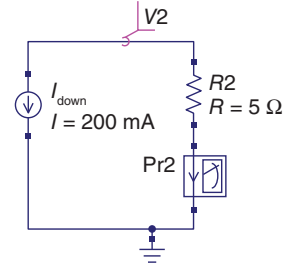In Figure 1.8, the current source arrow indicates counterclockwise circulation of current around the loop. The meter, pointing the same direction in Figure 1.8 as it does in Figure 1.7, indicates opposite circulation direction from the current source and correspondingly the current measured under Pr2.1 is negative 0.2 A.



Number	Pr2.1	V2.V
1	-0.2	-1

Figure 1.7 Circuit simulation schematic with a DC current source, pointed down, and a resistor.

1.1.2.3 Reference Polarity versus Physical Current Flow Direction

It is important to distinguish between actual current flow direction and reference polarity. If we reversed the direction of the current meter in Figure 1.7, the simulation would indicate a positive current value for Pr2.1, but the current still flows counterclockwise in the circuit.

The arrow pointing down, in the current source in Figure 1.8, indicates positive current going down from the current source and then up through the resistor. Using the same + (plus) and - (minus) signs on the resistor as a reference polarity for the resistor, we would get a negative voltage.

In Figure 1.7 the reference direction for the current is down, indicated by an arrow, in both schematics (Figures 1.7 and 1.8). The current polarity will be measured relative to this counter clockwise reference direction.

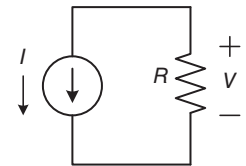


Figure 1.8 Schematic with a current source, pointed up, and a resistor.

1.2 Branch Relationships and I - V Characteristics

1.2.1 Circuit Element Branch Relationships

1.2.1.1 Ohm's Law is a Resistor's Branch Relationship

Ohm's law $V = IR$, describing the behavior of a resistor, is the branch relationship for a resistor. Figure 1.9 shows how voltage V can be expressed as a function of I (voltage as a dependent variable) or current can be expressed as a function of V (current as the dependent variable).

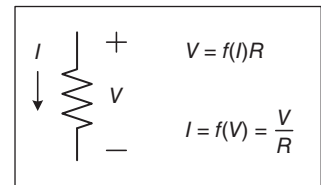


Figure 1.9 Resistor schematic diagram and ohm's law expressions where current or voltage are dependent.

1.2.1.2 Capacitor and Inductor Branch Relationships

The branch relationships for capacitors and inductors involve first derivatives and integrals, as shown in Figure 1.10. The branch relationships for capacitors and inductors will be studied in more detail in subsequent chapters on reactive elements.

Branch Relationships for R, L, and C



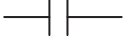
Circuit element	Current as a function of voltage	Voltage as a function of current
Resistor 	$I = \frac{V}{R}$	$V = IR$
Inductor 	$I = \frac{1}{L} \int_0^T V dt + I_0$	$V = L \frac{di}{dt}$
Capacitor 	$I = C \frac{dV}{dt}$	$V = \frac{1}{C} \int_0^T Idt + V_0$

Figure 1.10 Table showing schematic symbols and branch relationships for resistor, inductor, and capacitor.

A circuit elements' defining equation (model) typically describes the current through the element in terms of the voltage across the element.

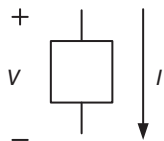


Figure 1.11a Fictitious generic circuit schematic symbol.

Figure 1.11a shows an example of a generic (non-specific) circuit element's schematic symbol, including a chosen sign convention for the voltage across it and the current through it.

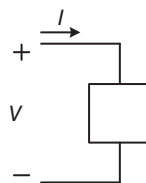


Figure 1.11b Fictitious generic circuit schematic symbol.

Drawn differently than Figure 1.11a, Figure 1.11b shows the same sign convention as Figure 1.11a for the voltage across a circuit element and the current through it that make up an I - V characteristic.

1.2.2 I - V Characteristic Plots

The branch relationship is sometimes called the I - V (current-voltage) characteristic of a circuit element. The I - V characteristic can be plotted with current on the vertical (dependent) axis and voltage on the horizontal (independent) axis. Some publications put voltage the vertical axis and current on the horizontal axis.

Resistors obeying Ohm's law are linear devices and this linearity appears as a straight line in the I - V characteristic.

1.2.2.1 I-V Characteristics for Circuit Elements

An *I-V* characteristic of a circuit element is the equation and graph of the current through the circuit element as a function of the voltage across the circuit element. (The shape of the curve in Figure 1.12 is a fictitious generic example.)

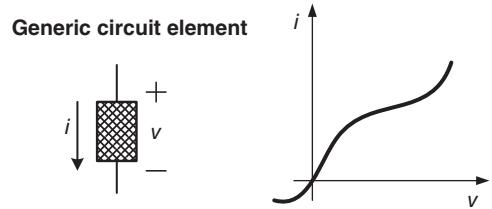


Figure 1.12 Fictitious generic circuit schematic symbol.

1.2.2.2 Resistor I-V Characteristic

A linear resistor's *I-V* characteristic is Ohm's law v equals iR . The *I-V* characteristic line, shown in Figure 1.13, is straight because there is a linear relationship between current and voltage. The slope of the line is 1 over R (1 over R equals G equals conductance).

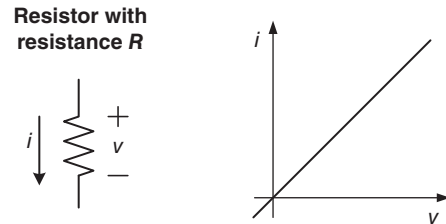


Figure 1.13 Resistor schematic symbol, marked with passive sign convention, adjacent to its linear *I-V* characteristic graph.

1.2.2.3 Non-resistor I-V Example

Diodes have a nonlinear exponential relationship between the voltage across them and the current through them, shown in Figure 1.14 and given by Equation 1.2.

$$i(v) = i_s e^{(qv/kT-1)} \tag{1.2}$$

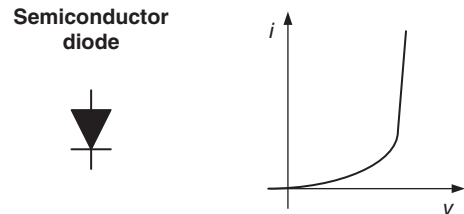


Figure 1.14 Diode schematic symbol and nonlinear *I/V* characteristic.

1.2.3 Circuit Elements Models and Schematic Symbols

1.2.3.1 Circuit Elements are Model Descriptions and Schematic Symbols

In electronics, a circuit element is a description (model) and a schematic symbol of a physical device in an electric or electronic circuit, as shown in Figure 1.15 for a resistor. Resistors, capacitors, inductors, opamps (operational amplifiers), transistors, and current sources are all examples of circuit elements. Branch relationships represent the defining model of a lumped circuit element such as a resistor, inductor, or diode.

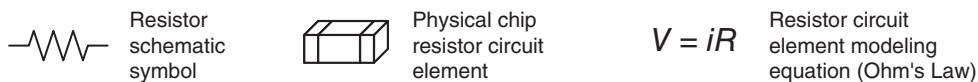


Figure 1.15 Resistor circuit element visual summary including the resistor schematic symbol, a drawing of a chip resistor, and Ohm's law, the branch relationship, and ideal lumped element modeling equation for a resistor.

1.2.3.2 Circuit Schematic Symbols

A circuit schematic symbol represents the circuit element in a schematic of the circuit, as shown in Figure 1.16.



Figure 1.16 Examples of common circuit element schematic symbols.

1.3 Ohm's Law, Resistance, and Resistors

1.3.1 Resistor and Conductor Equations

1.3.1.1 Resistors



Figure 1.17 Resistor schematic symbol.

A resistor, shown in Figure 1.17, is a circuit element which resists the flow of electrical current. An applied voltage is required in order to pass current through a resistor. The resistance R is the ratio of the voltage applied to the current that flows through the resistor. This ratio relationship is called Ohm's law. The unit of resistance is the ohm (Ω).

1.3.1.2 Ohm's Law

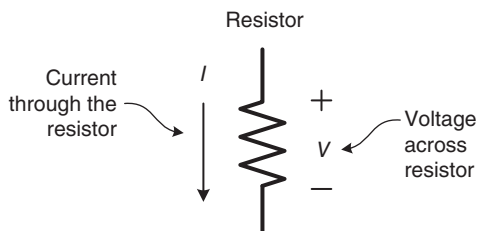


Figure 1.18 Resistor schematic symbol labeled with passive sign convention for visualizing Ohm's law.

Ohm's law states that the voltage across a resistor, shown in Figure 1.18, equals the current through the resistor times the resistance R of the resistor.

Equivalently, Ohm's law states that the current through the resistor equals the voltage across the resistor divided by the resistance R .

$$V = IR \quad (1.3)$$

$$IG = \frac{V}{R} = GV \quad (1.4)$$

$$R = \frac{V}{I} \quad (1.5)$$

Equations 1.3, 1.4, and 1.5 are all statements of Ohm's law, which describes the behavior of a resistor. V is the voltage across the resistor. I is the current through the resistor. R is the resistance and G is conductance, the inverse of resistance, shown in Equation 1.6. The unit of conductance is the siemen. It used to be called the mho.

Ohm's law assumes that the resistor is linear, that is, that the resistance of the resistor does not vary as a function of time, current, or voltage.

$$G = \frac{1}{R} = \frac{I}{V} \quad (1.6)$$

1.3.1.3 Ohm's Law Notation with Time-Dependent Functions

Ohm's law is also valid for currents and voltages that vary as a function of time. (But the resistance is still constant with respect to time, voltage, and current.)