



IEEE Press Series on Power and Energy Systems
Ganesh Kumar Venayagamoorthy, Series Editor

Control of Power Electronic Converters with Microgrid Applications

Arindam Ghosh, Firuz Zare




IEEE PRESS

WILEY

Table of Contents

[Cover](#)

[Series Page](#)

[Title Page](#)

[Copyright Page](#)

[Dedication Page](#)

[Author Biographies](#)

[Preface](#)

[Acknowledgments](#)

[1 Introduction](#)

[1.1 Introduction to Power Electronics](#)

[1.2 Power Converter Modes of Operation](#)

[1.3 Power Converter Topologies](#)

[1.4 Harmonics and Filters](#)

[1.5 Power Converter Operating Conditions, Modelling, and Control](#)

[1.6 Control of Power Electronic Systems](#)

[1.7 Power Distribution Systems](#)

[1.8 Concluding Remarks](#)

[References](#)

[2 Analysis of AC Signals](#)

[2.1 Symmetrical Components](#)

[2.2 Instantaneous Symmetrical Components](#)

[2.3 Harmonics](#)

[2.4 Clarke and Park Transforms](#)

[2.5 Phase Locked Loop \(PLL\)](#)

[2.6 Concluding Remarks](#)

[Problems](#)

[Notes and References](#)

[3 Review of SISO Control Systems](#)

[3.1 Transfer Function and Time Response](#)

[3.2 Routh-Hurwitz's Stability Test](#)

[3.3 Root Locus](#)

[3.4 PID Control](#)

[3.5 Frequency Response Methods](#)

[3.6 Relative Stability](#)

[3.7 Compensator Design](#)

[3.8 Discrete-time Control](#)

[3.9 Concluding Remarks](#)

[Problems](#)

[Notes and References](#)

[4 Power Electronic Control Design Challenges](#)

[4.1 Analysis of Buck Converter](#)

[4.2 Transfer Function of Boost Converter](#)

[4.3 Concluding Remarks](#)

[Problems](#)

[Notes and References](#)

[5 State Space Analysis and Design](#)

[5.1 State Space Representation of Linear Systems](#)

[5.2 Solution of State Equation of a Continuous-time System](#)

[5.3 Solution of State Equation of a Discrete-time System](#)

[5.4 Relation Between State Space Form and Transfer Function](#)

[5.5 Eigenvalues and Eigenvectors](#)

[5.6 Diagonalization of a Matrix Using Similarity Transform](#)

[5.7 Controllability of LTI Systems](#)

[5.8 Observability of LTI Systems](#)

[5.9 Pole Placement Through State Feedback](#)

[5.10 Observer Design \(Full Order\)](#)

[5.11 Control of DC-DC Converter](#)

[5.12 Concluding Remarks](#)

[Problems](#)

[Notes and References](#)

[6 Discrete-time Control](#)

[6.1 Minimum Variance \(MV\) Prediction and Control](#)

[6.2 Pole Placement Controller](#)

[6.3 Generalized Predictive Control \(GPC\)](#)

[6.4 Adaptive Control](#)

[6.5 Least-squares Estimation](#)

[6.6 Self-tuning Controller](#)

[6.7 Concluding Remarks](#)

[Problems](#)

[Notes and References](#)

[7 DC-AC Converter Modulation Techniques](#)

[7.1 Single-phase Bridge Converter](#)

[7.2 SPWM of Three-phase Bridge Converter](#)

[7.3 Space Vector Modulation \(SVM\)](#)

[7.4 SPWM with Third Harmonic Injection](#)

[7.5 Multilevel Converters](#)

[7.6 Concluding Remarks](#)

[Problems](#)

Notes and References

8 Control of DC-AC Converters

8.1 Filter Structure and Design

8.2 State Feedback Based PWM Voltage Control

8.3 State Feedback Based SVPWM Voltage Control

8.4 Sliding Mode Control

8.5 State Feedback Current Control

8.6 Output Feedback Current Control

8.7 Concluding Remarks

Problems

Notes and References

9 VSC Applications in Custom Power

9.1 DSTATCOM in Voltage Control Mode

9.2 Load Compensation

9.3 Other Custom Power Devices

9.4 Concluding Remarks

Problems

Notes and References

10 Microgrids

10.1 Operating Modes of a Converter

10.2 Grid Forming Converters

10.3 Grid Feeding Converters

10.4 Grid Supporting Converters for Islanded Operation of Microgrids

10.5 Grid-connected Operation of Microgrid

10.6 DC Microgrids

10.7 Integrated AC-DC System

10.8 Control Hierarchies of Microgrids

[10.9 Smart Distribution Networks: Networked Microgrids](#)

[10.10 Microgrids in Cluster](#)

[10.11 Concluding Remarks](#)

[Problems](#)

[Notes and References](#)

[11 Harmonics in Electrical and Electronic Systems](#)

[11.1 Harmonics and Interharmonics](#)

[11.2 Power Quality Factors and Definitions](#)

[11.3 Harmonics Generated by Power Electronics in Power Systems](#)

[11.4 Power Quality Regulations and Standards](#)

[11.5 Concluding Remarks](#)

[Notes and References](#)

[Index](#)

[IEEE Press Series on Power and Energy Systems](#)

[End User License Agreement](#)

List of Tables

Chapter 2

[Table 2.1 Values of the sequence vectors over a fundamental cycle.](#)

Chapter 3

[Table 3.1 The steady state error depending on the system type for different...](#)

[Table 3.2 The selection of PID parameters.](#)

Chapter 4

[Table 4.1 Buck converter design parameters.](#)

[Table 4.2 Boost converter parameters.](#)

Chapter 6

[Table 6.1 List of different stochastic processes.](#)

[Table 6.2 Estimated values for different total number of samples.](#)

[Table 6.3 RLS algorithm.](#)

Chapter 7

[Table 7.1 Eight switching states of a three-phase converter.](#)

[Table 7.2 Timing information for the six regions.](#)

[Table 7.3 Switching information for the six regions.](#)

[Table 7.4 Switching states for a three-level, single-phase diode-clamped co...](#)

[Table 7.5 Only possible switching states for a three-level, three-phase dio...](#)

[Table 7.6 Switching states for a three-level, single-phase flying capacitor...](#)

Chapter 8

[Table 8.1 System parameters for Example 8.7.](#)

Chapter 9

[Table 9.1 Parameters of the system of Figure 9.1.](#)

Chapter 10

[Table 10.1 Steady state quantities obtained for the resistive grid.](#)

[Table 10.2 Steady state quantities obtained in Example 10.8.](#)

[Table 10.3 System parameters chosen for Example 10.8.](#)

[Table 10.4 Operating scenarios of series connected microgrids to a single f...](#)

[Table 10.5 Operating scenarios of parallel connected microgrids to a single...](#)

[Table 10.6 PFC operation.](#)

[Table 10.7 Dynamic droop gains of Microgrid-3 in Example 10.20.](#)

Chapter 11

[Table 11.1 Odd harmonics limits in percentage of demand load current \(\$I_L\$](#)

[Table 11.2 Harmonic limits based on IEEE 1547.](#)

[Table 11.3 Recommended MVDC voltage classes.](#)

[Table 11.4 Proposed rated withstand voltages for MVDC voltage classes.](#)

List of Illustrations

Chapter 1

[Figure 1.1 Schematic diagram of a power electronic circuit.](#)

[Figure 1.2 The main active and passive components used in controllers and ga...](#)

[Figure 1.3 The main active and passive components used in power converters....](#)

[Figure 1.4 Four different configurations of power converters: \(a\) DC-DC, \(b\)...](#)

[Figure 1.5 \(a\) Power converter supplying a load and \(b\) four quadrants of op...](#)

[Figure 1.6 \(a\) Power converter in unidirectional power flow and \(b\) two mode...](#)

[Figure 1.7 \(a\) Power converter in bidirectional power flow and \(b\) four mode...](#)

[Figure 1.8 Power converter topologies: \(a\) and \(b\). low-frequency diode recti...](#)

[Figure 1.9 \(a\) A DC-DC converter, \(b\) its modulated signal, and \(c\) the outp...](#)

[Figure 1.10 \(a\) A diode rectifier connected to a DC-AC converter and \(b\) vol...](#)

[Figure 1.11 A general block diagram of a power electronic system with differ...](#)

[Figure 1.12 Operating conditions of DC-DC converters.](#)

[Figure 1.13 The time domain behavior of inductor current of a DC-DC converte...](#)

[Figure 1.14 \(a\) A buck converter, \(b\) when the switch is turned ON, and \(c\) ...](#)

[Figure 1.15 \(a\) Open-loop control system and \(b\) feedback control system.](#)

[Figure 1.16 \(a\) Open-loop control system, feedback control system \(b\) with \$\alpha\$...](#)

[Figure 1.17 The response of the nonlinear system with three different values...](#)

[Figure 1.18 \(a\) A radial distribution system, \(b\) phasor diagram when the ca...](#)

Chapter 2

[Figure 2.1 Trace of \(a\) a positive sequence and \(b\) a negative sequence over...](#)

[Figure 2.2 Trace of \(a\) a positive sequence and \(b\) a negative sequence over...](#)

[Figure 2.3 Estimated \(a\) magnitude and \(b\) phase of the phasor sequence comp...](#)

[Figure 2.4 Estimated and actual waveforms for the three phases.](#)

[Figure 2.5 Estimated fundamental and actual distorted waveforms for the thre...](#)

[Figure 2.6 Instantaneous real and reactive power. \(a\) Active power, \(b\) reac...](#)

[Figure 2.7 \(a\) Distorted voltage waveform and \(b\) its harmonic spectrum.](#)

[Figure 2.8 \(a\) Clarke and \(b\) Park transform of a balanced three-phase volta...](#)

[Figure 2.9 \(a\) Clarke and \(b\) inverse Clarke transform of unbalanced voltage...](#)

[Figure 2.10 A simple radial system.](#)

[Figure 2.11 Simulation results of the circuit of Figure 2.10 using instantan...](#)

[Figure 2.12 \(a\) \$\alpha\beta\$ components, \(b\) the angle \$\theta\$, and \(c\) dq components o...](#)

[Figure 2.13 Schematic diagram of a PLL.](#)

[Figure 2.14 Block diagram of a three-phase PLL.](#)

[Figure 2.15 Linearized block diagram of the three-phase PLL.](#)

[Figure 2.16 PLL performance: \(a\) reference voltage, \(b\) synthesized current,...](#)

[Figure 2.17 Block diagram of a PLL for unbalanced voltages.](#)

[Figure 2.18 Performance of PLL for unbalanced signals: \(a\) reference voltage...](#)

[Figure 2.19 Frequency estimation in \$\alpha\beta\$ components: \(a\) angle error, \(b\) PI c...](#)

[Figure P2.1 Circuit of Problem 2.1.](#)

[Figure P2.2 Open delta circuit of Problem 2.2.](#)

[Figure P2.3 Distribution system supplying unbalanced load of Problem 2.3.](#)

[Figure P2.4 Distribution system for VU calculation of Problem 2.4.](#)

Chapter 3

[Figure 3.1 Block diagram of a closed-loop system.](#)

[Figure 3.2 Step response of a second-order system: \(a\) undamped, \(b\) underda...](#)

[Figure 3.3 \(a\) An RLC circuit and \(b\) its step response.](#)

[Figure 3.4 Step response of a first-order system with two different values o...](#)

[Figure 3.5 Step response of a third-order system with two different values o...](#)

[Figure 3.6 Root locus plot of the system of Example 3.4.](#)

[Figure 3.7 Root locus on the real axis.](#)

[Figure 3.8 \(a, b and c\) Root locus plots for the three cases of Example 3.5....](#)

[Figure 3.9 Root locus plot for the system of Example 3.6.](#)

[Figure 3.10 \(a\) Root locus plot for the system of Example 3.7 and \(b\) zoomed...](#)

[Figure 3.11 Block diagram of the PID control of a unity feedback system.](#)

[Figure 3.12 Root locus plot for the system of Example 3.8.](#)

[Figure 3.13 Step response with two different values of integral gain in Exam...](#)

[Figure 3.14 Step response of the system of Example 3.9 with \(a\) no controlle...](#)

[Figure 3.15 \(a\) Sustained oscillation time period and \(b\) step response of t...](#)

[Figure 3.16 The magnitude plots of \(a\) the gain and \(b\) the integral terms....](#)

[Figure 3.17 The magnitude plots \(a\) the first- and \(b\) the second-order term...](#)

[Figure 3.18 The phase plots of \(a\) the first- and \(b\) second-order terms.](#)

[Figure 3.19 The composite Bode plot of Examples 3.11 and 3.12.](#)

[Figure 3.20 Nyquist plot of the transfer function given in \(3.45\).](#)

[Figure 3.21 Nyquist path \(a\) without a singularity on the \$j\omega\$ axis and \(...\)](#)

[Figure 3.22 Polar plots in two different planes: \(a\) \$F\(j\omega\) = 1 + G\(j\omega...\$](#)

[Figure 3.23 Nyquist plot of the system of Example 3.13.](#)

[Figure 3.24 Nyquist plot for the \(a\) undamped system and \(b\) stable system o...](#)

[Figure 3.25 Nyquist plots as the open-loop gain \$|GH|\$ of a unity feedback sys...](#)

[Figure 3.26 Nyquist plot of a system with \(a\) positive phase and GMs and \(b\)...](#)

[Figure 3.27 Bode plot of a system with \(a\) positive phase and GMs and \(b\) ne...](#)

[Figure 3.28 Bode plot for the system designed in Example 3.15.](#)

[Figure 3.29 Bode plot of the compensated system of Example 3.16.](#)

[Figure 3.30 Step response of the compensated system of Example 3.16.](#)

[Figure 3.31 Bode plot showing bandwidth and cutoff frequency.](#)

[Figure 3.32 Log magnitude of a first-order system. \(a\) gain plot and \(b\) gai...](#)

[Figure 3.33 Step response of the system of Example 3.17 for three different ...](#)

[Figure 3.34 \(a\) Polar plot and \(b\) Bode plot of a lead compensator.](#)

[Figure 3.35 Bode plot of the uncompensated system of Example 3.18.](#)

[Figure 3.36 Bode plot of the compensated system of Example 3.18.](#)

[Figure 3.37 The closed-loop step response of the compensated system of Examp...](#)

[Figure 3.38 Bode plot of the lag compensator with \$\beta = 10\$ and \$\tau = 0...\$](#)

[Figure 3.39 Bode plot of a lead-lag compensator with \$\beta = 10\$, \$\tau_1 = ...\$](#)

[Figure 3.40 Schematic diagram of a digital control system.](#)

[Figure 3.41 The sampling process: \(a\) ideal sampler and \(b\) impulse modulate...](#)

[Figure 3.42 Stable and unstable operating regions on the z-plane.](#)

[Figure P3.1 OPAMP circuit of Problem 3.1.](#)

[Figure P3.2 Unity feedback control system of Problem 3.2.](#)

[Figure P3.3 Root locus for Problem 3.3.](#)

[Figure P3.8 Feedback system of Problem 3.8.](#)

Chapter 4

[Figure 4.1 The block diagram of a DC-DC converter connected to two different...](#)

[Figure 4.2 The circuit diagram of a buck converter connected to a battery \(\$v\$](#)

[Figure 4.3 The circuit diagram of a buck converter when the switch is \(a\) on...](#)

[Figure 4.4 Voltage and current waveforms of a buck converter over a switchin...](#)

[Figure 4.5 Capacitor current and voltage waveforms.](#)

[Figure 4.6 Initial starting transients of the buck converter.](#)

[Figure 4.7 Steady state voltage and current ripples with the buck converter....](#)

[Figure 4.8 System behavior for a load change when the buck converter is supp...](#)

[Figure 4.9 Voltage and current behavior when the buck converter is supplied ...](#)

[Figure 4.10 Circuit diagrams of a buck converter with negative feedback and ...](#)

[Figure 4.11 \(a\) Sawtooth and control waveforms and \(b\) transfer function of ...](#)

[Figure 4.12 Root locus plot of the small signal model of the buck converter...](#)

[Figure 4.13 Dynamic response of the buck converter small signal model to P-t...](#)

[Figure 4.14 Closed-loop control of a DC-DC converter.](#)

[Figure 4.15 Output voltage response and duty ratio of the buck converter.](#)

[Figure 4.16 \(a\) A boost converter, its equivalent circuit when the switch is...](#)

[Figure 4.17 Root locus plot of the boost converter.](#)

[Figure 4.18 Root locus plot of the boost converter when \$K_I\$ increases from 0 ...](#)

[Figure 4.19 Boost converter response with PI controller.](#)

[Figure 4.20 \(a\) Two-loop control of boost converter, \(b\) inner current loop,...](#)

[Figure 4.21 Bode plot of the uncompensated current loop.](#)

[Figure 4.22 Bode plot of the lag compensator.](#)

[Figure 4.23 Bode plot of the compensated current loop.](#)

[Figure 4.24 Bode plot of the compensated voltage loop.](#)

[Figure 4.25 Response of the two-loop control system.](#)

[Figure 4.26 Boost converter with stray components.](#)

Chapter 5

[Figure 5.1 Step response of the system of Example 5.15 with two different va...](#)

[Figure 5.2 Continuous-time state feedback with integral control.](#)

[Figure 5.3 System response with state feedback with integral control.](#)

[Figure 5.4 System response with different locations of the fourth pole. \(a\) ...](#)

[Figure 5.5 System response with LQR for two values of control weighting. \(a\)...](#)

[Figure 5.6 Structure of feedback controller with observer.](#)

[Figure 5.7 System response with state feedback control and observer.](#)

[Figure 5.8 \(a\) The schematic diagram of a boost converter and its equivalent...](#)

[Figure 5.9 Switching scheme of DC-DC converters based on duty ratio control....](#)

[Figure 5.10 Steady state voltage and current waveforms of a boost converter....](#)

[Figure 5.11 Feedback control structure of DC-DC converter.](#)

[Figure 5.12 Boost converter response when averaged values are used in feedba...](#)

[Figure 5.13 Boost converter response when instantaneous values are used in f...](#)

[Figure 5.14 Boost converter response with state feedback control without the...](#)

[Figure 5.15 Eigenvalue plot as the load resistance changes.](#)

[Figure 5.16 Boost converter response for a large change in the output resist...](#)

[Figure P5.1 The circuit diagram of Problem 5.1.](#)

[Figure P5.13 Schematic diagram of a buck-boost converter.](#)

Chapter 6

[Figure 6.1 System output and input for the three-step-ahead MV control of Ex...](#)

[Figure 6.2 System output and input for the one-step-ahead MV control of Exam...](#)

[Figure 6.3 System output and input for unrestricted control of Example 6.6....](#)

[Figure 6.4 System output and input for restricted bang-bang control of Examp...](#)

[Figure 6.5 Block diagram of the pole placement controller.](#)

[Figure 6.6 System output and input for the three-step-ahead pole placement c...](#)

[Figure 6.7 Radial shifting of poles in the z-plane.](#)

[Figure 6.8 System response with pole shift control for two different values ...](#)

[Figure 6.9 System response with pole shift control for the nonminimum phase ...](#)

[Figure 6.10 System response with GPC of Example 6.7.](#)

[Figure 6.11 Typical SISO system with a disturbance input.](#)

[Figure 6.12 Model reference adaptive control.](#)

[Figure 6.13 Self-tuning adaptive control.](#)

[Figure 6.14 The actual length of fall and the measured length of fall.](#)

[Figure 6.15 The system response to a unit step input.](#)

[Figure 6.16 Identified parameters and identifier residuals. \(a\) Estimate \(\$\theta...\$](#)

[Figure 6.17 Identified parameters and identifier residuals. \(a\) Estimate \(\$\theta...\$](#)

[Figure 6.18 System output and identified parameters for the MV self-tuning c...](#)

[Figure 6.19 System output and identified parameters for the self-tuning cont...](#)

[Figure 6.20 System output and identified parameters for the poles shift self...](#)

[Figure 6.21 Boost converter \(a\) output voltage, \(b\) inductor current, and \(c...](#)

[Figure 6.22 Estimated parameters of the boost converter during load changes....](#)

Chapter 7

[Figure 7.1 Single-phase VSC circuit: \(a\) equivalent representation, \(b\) swit...](#)

[Figure 7.2 Reference current and upper and lower hysteresis bands.](#)

[Figure 7.3 Steady state voltage and current waveforms of an H-bridge convert...](#)

[Figure 7.4 Current tracking performance of H-bridge converter with different...](#)

[Figure 7.5 Converter output current and voltage with a high load. \(a\) Output...](#)

[Figure 7.6 Undermodulated bipolar SPWM and converter output voltage.](#)

[Figure 7.7 Overmodulated bipolar SPWM and converter output voltage.](#)

[Figure 7.8 Rms values of the fundamental components of the output voltage fo...](#)

[Figure 7.9 Undermodulated unipolar SPWM and converter output voltage. \(a\) Ca...](#)

[Figure 7.10 Three-phase converter circuits: \(a\) bridge converter and \(b\) neu...](#)

[Figure 7.11 Structure of \(a\) transformer couple of three H-bridge converters...](#)

[Figure 7.12 Converter connected to a back emf through an RL impedance.](#)

[Figure 7.13 SPWM control of a three-phase converter: \(a\) carrier and referen...](#)

[Figure 7.14 Output current with three different frequencies of the carrier w...](#)

[Figure 7.15 The converter structure and the switching states.](#)

[Figure 7.16 The converter output voltage vector space.](#)

[Figure 7.17 Placement of vector \$v_P\$ in \(a\) Region-1 between vectors \$V_1\$ an...](#)

[Figure 7.18 Switching patterns in six regions: \(a\) Region-1, \(b\) Region-2, \(...](#)

[Figure 7.19 Variation in angle of the vector \$V_P\$ and the computation of th...](#)

[Figure 7.20 Switching signals and the output currents in Example 7.4.](#)

[Figure 7.21 Modulating wave for two different values of \$A\$. \(a\) For \$A = -1/3\$...](#)

[Figure 7.22 Modulating wave for two different values of \$K\$.](#)

[Figure 7.23 Line to neutral voltage for two different values of \$K\$.](#)

[Figure 7.24 \(a\) Schematic diagram of multilevel converter and \(b\) output vol...](#)

[Figure 7.25 Output voltage waveform and harmonic spectrum of \(a\) two-level c...](#)

[Figure 7.26 \(a\) One leg of a three-level diode-clamped converter, \(b\) its ou...](#)

[Figure 7.27 The current loops when \$S_{a1} = 0\$ and \$S_{a2} = 0\$ for \(a\) positive ...](#)

[Figure 7.28 The current loops when \$S_{a1} = 0\$ and \$S_{a2} = 1\$ for \(a\) positive ...](#)

[Figure 7.29 The current loops when \$S_{a1} = 1\$ and \$S_{a2} = 1\$ for \(a\) positive ...](#)

[Figure 7.30 The current loops when \$S_{a1} = 1\$ and \$S_{a2} = 0\$ for \(a\) positive ...](#)

[Figure 7.31 Three-level diode-clamped multilevel converter: \(a\) single-phase...](#)

[Figure 7.32 \(a\) One leg of a three-level flying capacitor converter, \(b\) its...](#)

[Figure 7.33 The current loops when \$S_{a1} = 0\$ and \$S_{a2} = 0\$ for \(a\) positive ...](#)

[Figure 7.34 The current loops when \(a\) \$S_{a1} = 0\$ and \$S_{a2} = 1\$ and \(b\) \$S_{a1}\$](#)

[Figure 7.35 The current loops when \$S_{a1} = 1\$ and \$S_{a2} = 1\$ for \(a\) positive ...](#)

[Figure 7.36 Three-level flying capacitor converter: \(a\) single-phase and \(b\)...](#)

[Figure 7.37 Schematic diagram of a three-phase cascaded multilevel converter...](#)

[Figure 7.38 \(a\) Schematic diagram of an MMC and \(b and c\) two possible SM st...](#)

[Figure 7.39 PD-PWM of a five-level converter: \(a\) carrier and modulating wav...](#)

[Figure 7.40 APOD-PWM of a five-level converter: \(a\) carrier and modulating w...](#)

[Figure 7.41 POD-PWM of a five-level converter: \(a\) carrier and modulating wa...](#)

Chapter 8

[Figure 8.1 \(a\) Single-phase voltage source converter with L filter; converte...](#)

[Figure 8.2 Bode plot of the LC filter.](#)

[Figure 8.3 Passive damping LCL filters: \(a\) series damper, \(b\) shunt RC damp...](#)

[Figure 8.4 Schematic diagram of \(a\) a voltage source converter with its outp...](#)

[Figure 8.5 Two different feedback control structures: \(a\) full state feedbac...](#)

[Figure 8.6 Bode plot of the HPF.](#)

[Figure 8.7 Tracking performance of the closed-loop system of Example 8.2.](#)

[Figure 8.8 Control signals in Example 8.2.](#)

[Figure 8.9 Feedback control structure with current observer.](#)

[Figure 8.10 Tracking performance of the closed-loop system of Example 8.3.](#)

[Figure 8.11 \(a\) Estimated and \(b\) actual phase-a current \$i_{1a}\$ of Example 8....](#)

[Figure 8.12 SVPWM feedback control structure.](#)

[Figure 8.13 Tracking performance of the closed-loop system of Example 8.4.](#)

[Figure 8.14 Switching signals of SVPWM control of Example 8.4.](#)

[Figure 8.15 H-bridge VSC with LC filter connected to a back emf.](#)

[Figure 8.16 Tracking performance with sliding mode control H-bridge converte...](#)

[Figure 8.17 Tracking performance with sliding mode control of three-phase co...](#)

[Figure 8.18 VSC in current control mode through an LCL filter.](#)

[Figure 8.19 Current tracking state feedback control structure.](#)

[Figure 8.20 Performance of the state feedback based current controller. \(a\)...](#)

[Figure 8.21 Current tracking failure due to hysteresis current control for V...](#)

[Figure 8.22 Current tracking output feedback control structure.](#)

[Figure 8.23 Performance of the output feedback based current controller.](#)

Chapter 9

[Figure 9.1 Single-line diagram of a radial system supplying two loads.](#)

[Figure 9.2 The loads currents in Example 9.1.](#)

[Figure 9.3 Three-leg DSTATCOM structure.](#)

[Figure 9.4 DSTATCOM structure with four H-bridges.](#)

[Figure 9.5 Four-leg DSTATCOM structure.](#)

[Figure 9.6 The distribution system of Figure 9.1 compensated by a DSTATCOM....](#)

[Figure 9.7 Firing pulse generation for discrete-time control.](#)

[Figure 9.8 The DC voltage, load angle, and PCC powers in Example 9.2 when th...](#)

[Figure 9.9 PCC voltages and load \$Z_1\$ currents in Example 9.9 when the DSTATC...](#)

[Figure 9.10 DC capacitor voltage and PCC voltage angle and PCC voltages with...](#)

[Figure 9.11 DC capacitor voltage and PCC voltage angle and PCC voltages with...](#)

[Figure 9.12 The DC voltage, load angle, and PCC voltage with a four-leg DSTA...](#)

[Figure 9.13 Neutral reference and actual current and current tracking error ...](#)

[Figure 9.14 Two sources connected through an inductance.](#)

[Figure 9.15 Power received at the receiving end for two different values of ...](#)

[Figure 9.16 DC bus voltage and PCC voltage angle during frequency mismatch. ...](#)

[Figure 9.17 DSTATCOM performance with frequency estimation algorithm.](#)

[Figure 9.18 The DC voltage and load angle with the power factor correcting f...](#)

[Figure 9.19 The PCC voltage magnitude and injected reactive power with the p...](#)

[Figure 9.20 Classical load compensator: \(a\) uncompensated and \(b\) compensate...](#)

[Figure 9.21 Schematic diagram of a load compensator circuit using a DSTATCOM...](#)

[Figure 9.22 \(a\) Load currents, \(b\) load currents, and \(c\) source voltage and...](#)

[Figure 9.23 \(a\) Average DC capacitor voltage and \(b\) average load power and ...](#)

[Figure 9.24 A DVR protecting a sensitive load.](#)

[Figure 9.25 Schematic diagram of a distribution system where a DVR protectin...](#)

[Figure 9.26 \(a\) Polluting load current, \(b\) PCC voltage, and \(c\) sensitive l...](#)

[Figure 9.27 Schematic diagram of a UPQC.](#)

[Figure P9.1 DSTATCOM compensated distribution system of Problems 9.1 and 9.2...](#)

[Figure P9.3 DSTATCOM compensated distribution system of Problem 9.3.](#)

[Figure P9.4 Series compensated distribution system of Problem 9.4.](#)

[Figure P9.5 Open-delta connection for Problem 9.4.](#)

Chapter 10

[Figure 10.1 Thematic diagram of a microgrid.](#)

[Figure 10.2 Schematic diagram of a typical microgrid.](#)

[Figure 10.3 Grid-connected VSC operation modes: \(a\) grid forming, \(b\) grid f...](#)

[Figure 10.4 Block diagram of closed-loop voltage control for grid forming co...](#)

[Figure 10.5 d- and q-axis voltages for grid forming converter with voltage f...](#)

[Figure 10.6 Phase voltages for grid forming converter with voltage feedback....](#)

[Figure 10.7 Block diagram for inner current and outer voltage of grid formin...](#)

[Figure 10.8 d- and q-axis voltages for grid forming converter with two loop ...](#)

[Figure 10.9 Phase voltages for grid forming converter with two loop controls...](#)

[Figure 10.10 Block diagram of the state feedback control structure of grid f...](#)

[Figure 10.11 d- and q-axis voltages for grid forming converter with state fe...](#)

[Figure 10.12 Phase voltages for grid forming converter with state feedback c...](#)

[Figure 10.13 Performance of the grid feeding converter.](#)

[Figure 10.14 Battery-connected grid feeding converter in a distribution netw...](#)

[Figure 10.15 \(a\) Power flow in the network and \(b\) current tracking error wh...](#)

[Figure 10.16 Two AC source connected together through a feeder.](#)

[Figure 10.17 Droop characteristics for inductive grid: \(a\) P-f droop and \(b\)...](#)

[Figure 10.18 P-f droop lines of a two-DG microgrid.](#)

[Figure 10.19 A simple microgrid with two DERs.](#)

[Figure 10.20 Microgrid operation results while operating with P-f and Q-V dr...](#)

[Figure 10.21 Droop characteristics for resistive grid: \(a\) Q-f droop and \(b\)...](#)

[Figure 10.22 Microgrid operation results while operating with Q-f and P-V dr...](#)

[Figure 10.23 Microgrid operation results while operating with combined droop...](#)

[Figure 10.24 Microgrid operation results while operating with P-f and Q-V dr...](#)

[Figure 10.25 Microgrid operation results while operating with Q-f and P-V dr...](#)

[Figure 10.26 Operation of islanded microgrid with a grid feeding converter....](#)

[Figure 10.27 Microgrid structure for angle droop control.](#)

[Figure 10.28 \(a\) Real and \(b\) reactive power supplied by the DERs, when oper...](#)

[Figure 10.29 Bus voltage \(a\) magnitude and \(b\) angle when the microgrid oper...](#)

[Figure 10.30 Schematic diagram of a utility connected microgrid.](#)

[Figure 10.31 Operation of a microgrid, when connected to a utility and subse...](#)

[Figure 10.32 Schematic diagram of power flow control between utility and mic...](#)

[Figure 10.33 The basic building blocks of a DCMG system.](#)

[Figure 10.34 Schematic diagram of a simple DCMG.](#)

[Figure 10.35 The effect of line resistance on the output voltage, power, and...](#)

[Figure 10.36 Schematic diagram of a DCMG containing buck and boost converter...](#)

[Figure 10.37 Performance of DCMG with \(a and b\) P-V and \(c and d\) I-V droop ...](#)

[Figure 10.38 Schematic diagram of a utility connected DCMG.](#)

[Figure 10.39 Schematic diagram of \(a\) DAB and \(b\) its equivalent circuit.](#)

[Figure 10.40 \(a\) Switching configuration of a DAB and its equivalent circuit...](#)

[Figure 10.41 Performance of utility connected DCMG. \(a\) Power flow in DCMG \(...\)](#)

[Figure 10.42 Three-level control structure of microgrids.](#)

[Figure 10.43 MAS-based distributed secondary control structure of a microgrid...](#)

[Figure 10.44 Serial microgrids on a single feeder.](#)

[Figure 10.45 Parallel microgrids on a single feeder.](#)

[Figure 10.46 Interconnected microgrids on multiple feeders.](#)

[Figure 10.47 Power flow and frequency before and after the interconnection o...](#)

[Figure 10.48 VSC-2 control scheme.](#)

[Figure 10.49 Microgrid power shortfall being supplied by utility in Example ...](#)

[Figure 10.50 Microgrid cluster formation through the PEH.](#)

[Figure 10.51 Future distribution grid with different types of networked microgrids...](#)

[Figure 10.52 \(a\) Structure of islanded microgrid cluster and \(b\) configuration...](#)

[Figure 10.53 Schematic diagram of a three-microgrid cluster.](#)

[Figure 10.54 Overload prevention scheme through controlled DC voltage genera...](#)

[Figure 10.55 Dynamic droop gain selection scheme.](#)

[Figure 10.56 Dynamic droop gain selection in power flow control scheme.](#)

[Figure 10.57 Microgrid-3 overload prevention: \(a\) required power to be drawn...](#)

[Figure 10.58 Power flow through \(a\) Microgrid-3 and \(b\) DC-PEH in Example 10...](#)

[Figure 10.59 DC capacitor voltage of the ICs of the three microgrids in Exam...](#)

[Figure 10.60 \(a\) Power flow in Microgrid-3 and \(b\) power supplied by Microgr...](#)

[Figure 10.61 \(a\) Power supply range in Microgrid-3 and \(b\) its dynamic droop...](#)

[Figure P10.3 The autonomous microgrid operating under angle droop of Problem...](#)

[Figure P10.5 Grid-connected microgrid of Problem 10.5.](#)

[Figure P10.9 Microgrid cluster of Problem 10.9.](#)

Chapter 11

[Figure 11.1 A load current waveform with harmonic and interharmonic componen...](#)

[Figure 11.2 Daily and hourly average values for 2-150 kHz voltage harmonics ...](#)

[Figure 11.3 Conducted and radiated EMI noise emission and propagation.](#)

[Figure 11.4 Common mode and differential mode current paths.](#)

[Figure 11.5 Common mode and differential mode currents in a motor drive syst...](#)

[Figure 11.6 Grid impedance impact on voltage harmonics in a distribution net...](#)

[Figure 11.7 Distortion in current due to different harmonic components.](#)

[Figure 11.8 Several harmonic mitigation techniques: \(a\) passive inductive fi...](#)

[Figure 11.9 Circuit diagram of a typical power electronic system.](#)

[Figure 11.10 A general circuit diagram of a three-phase motor drive applicat...](#)

[Figure 11.11 \(a\) A three-phase diode rectifier with \(a\) DC link filter and i...](#)

[Figure 11.12 \(a\) The voltage output of a three-phase diode rectifier and \(b\)...](#)

[Figure 11.13 The extraction of the grid current based on the DC link current...](#)

[Figure 11.14 \(a\) The grid and \(b\) the rectifier voltage waveforms with diffe...](#)

[Figure 11.15 A single-phase diode rectifier \(a\) without a boost converter an...](#)

[Figure 11.16 \(a\) Current waveform of a single-phase diode rectifier without ...](#)

[Figure 11.17 \(a\) Current waveform of a single-phase diode rectifier with a b...](#)

[Figure 11.18 An AFE topology with current control and measuring units.](#)

[Figure 11.19 Block diagram of the closed-loop AFE control system.](#)

[Figure 11.20 A simplified model of an AFE system with a closed-loop control ...](#)

[Figure 11.21 A simplified model of a network with two different loads.](#)